

# Template Week 2 – Logic

Student number:

## Assignment 2.1: Parking lot

Which gates do you need?

AND gate

Complete this table

Parking lot 1	Parking lot 2	Parking lot 3	Result (full)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

## Assignment 2.2: Android or iPhone

Which gates do you need?

XOR gate

Complete this table

Android phone	iPhone	Result (Phone in possession)
0	0	0
0	1	1
1	0	1
1	1	0

### Assignment 2.3: Four NAND gates

Complete this table

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0


How can the design be simplified?

It's a XOR gate

### Assignment 2.4: Getting to know Logisim evolution

Screenshot of the design with your name and student number in it:


**Marco Vermaas 547518**

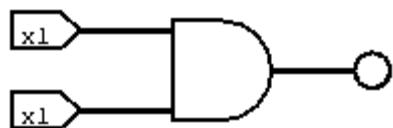

### Assignment 2.5: SR Latch


Screenshot SR Latch in Logisim with your name and student number:

**Marco Vermaas 547518**

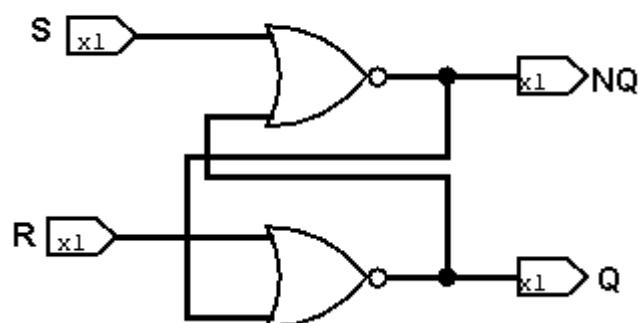
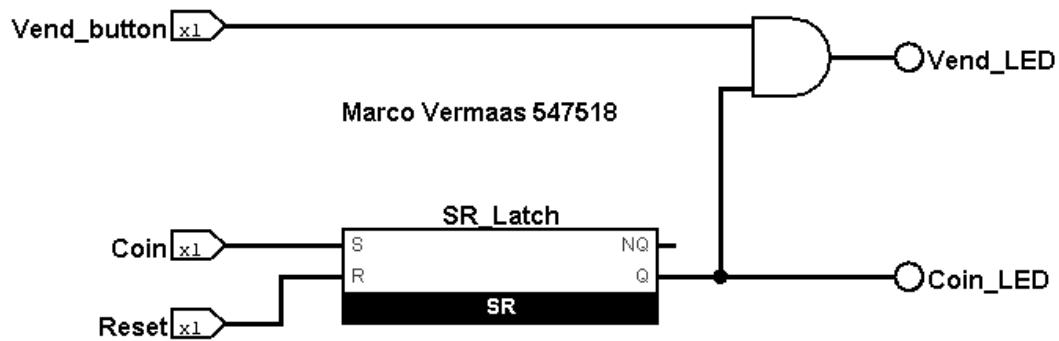
### Assignment 2.6: Vending Machine

Screenshot Vending Machine in Logisim with your name and student number:



### Assignment 2.7: Bitwise operators

Complete the java source code for bitwise operators. Put the source code here.

**1#**  
public class Main {  
 public static void main(String[] args) {  
 int number = 5;  
  
 if((number & 1) == 1) System.out.println("number is odd");  
 else System.out.println("number is even");  
 }  
}

**2#**  
public class test {  
  
 public static void main(String[] args) {  
  
 int number = 4;  
  
 if (number > 0 && (number & (number - 1)) == 0) {  
  
 System.out.println(number + " is a power of 2");  
 } else {  
  
 System.out.println(number + " is NOT a power of 2");  
 }  
 }  
}

**3#**

```
public class Main {  
    public static void main(String[] args) {  
        final int READ = 4;  
        final int WRITE = 2;  
        final int EXECUTE = 1;  
  
        int userPermissions = 7;  
  
        if ((userPermissions & READ) != 0) {  
            System.out.println("User has read permissions");  
        } else {  
            System.out.println("User can't read. No permissions.");  
        }  
    }  
}
```

**4#**

```
public class Main {  
    public static void main(String[] args) {  
        final int READ = 4;  
        final int WRITE = 2;  
        final int EXECUTE = 1;  
  
        int userPermissions = 0;  
  
        userPermissions = userPermissions | READ | EXECUTE;  
  
        System.out.println("User permissions: " + userPermissions);  
    }  
}
```

**5#**

```
public class Main {  
    public static void main(String[] args) {  
        final int READ = 4;  
        final int WRITE = 2;  
        final int EXECUTE = 1;  
  
        int userPermissions = 6;  
  
        userPermissions = userPermissions ^ WRITE;  
  
        System.out.println("User permissions: " + userPermissions);  
    }  
}
```

```

6#
public class test {
    public static void main(String[] args) {
        int number = 5;

        number = ~number + 1;

        System.out.println("Number: " + number);
    }
}

```

### **Assignment 2.8: Java Application Bit Calculations**

Create a java program that accepts user input and presents a menu with options.

1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Keep this application because you need to expand it in week 6 for calculating network segments.

Paste source code here, with a screenshot of a working application.

```

import java.util.Scanner;

public class Main {
    public static void main(String[] args) {
        Scanner scanner = new Scanner(System.in);
        int number;

        System.out.print("Enter a number: ");
        number = scanner.nextInt();

        int choice;
        do {
            System.out.println("\n--- Menu ---");
            System.out.println("1. Is number odd?");
            System.out.println("2. Is number a power of 2?");
            System.out.println("3. Two's complement of number?");
            System.out.println("4. Exit");
            System.out.print("Choose an option: ");
            choice = scanner.nextInt();

            switch (choice) {
                case 1:
                    if ((number & 1) == 1) {

```

```

        System.out.println(number + " is odd");
    } else {
        System.out.println(number + " is even");
    }
    break;

case 2:
    if (number > 0 && (number & (number - 1)) == 0) {
        System.out.println(number + " is a power of 2");
    } else {
        System.out.println(number + " is NOT a power of 2");
    }
    break;

case 3:
    System.out.println("Two's complement of " + number + " is: " + (number = ~number + 1));
    break;

case 4:
    System.out.println("Exiting...");
    break;

default:
    System.out.println("Invalid choice. Try again.");
    break;
}

} while (choice != 4);

scanner.close();
}
}

```

Ready? Then save this file and export it as a pdf file with the name: [week2.pdf](#)